




CLAP / SOUND CONTROLLED SWITCH FOR PHYSICALLY DISABLED PERSONS

BY:

927624BEC154(PON SANMUGA VISHAL G)
927624BEC139(MUTHURAJ R)
927624BEC140(MYTHEESH M)
927624BEC148(NISHANTH AMUTHAN V)





PROBLEM STATEMENT AND SOLUTION

PROBLEM STATEMENT:

Many physically disabled individuals face difficulty in operating manual switches for electrical appliances.

SOLUTION :

Design a sound-activated switch using Microphone to detect clap/sound.




PROJECT GOALS

- 1) No physical contact, cost-effective, easy to implement.
- 2) Relay driver to control appliances
- 3) Able achieve idependency in operating machineries.


COMPONENTS

- 1) Microphone module
- 2) 5v relay
- 3) Arduino
- 4) Connecting Wires
- 5) Comparator(LM393)
- 6) potentiometer


CIRCUIT DIAGRAM

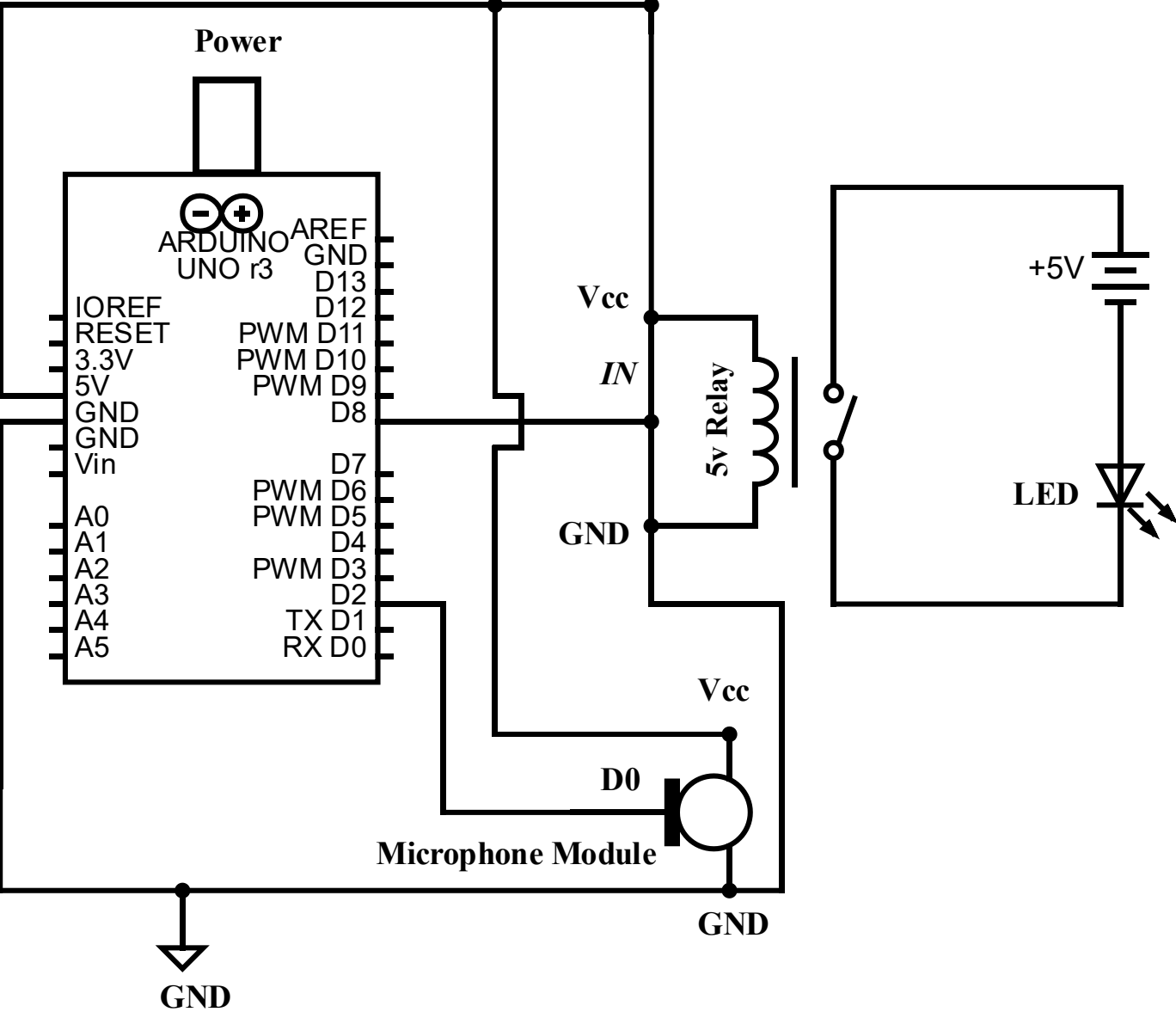

MICROPHONE MODULE

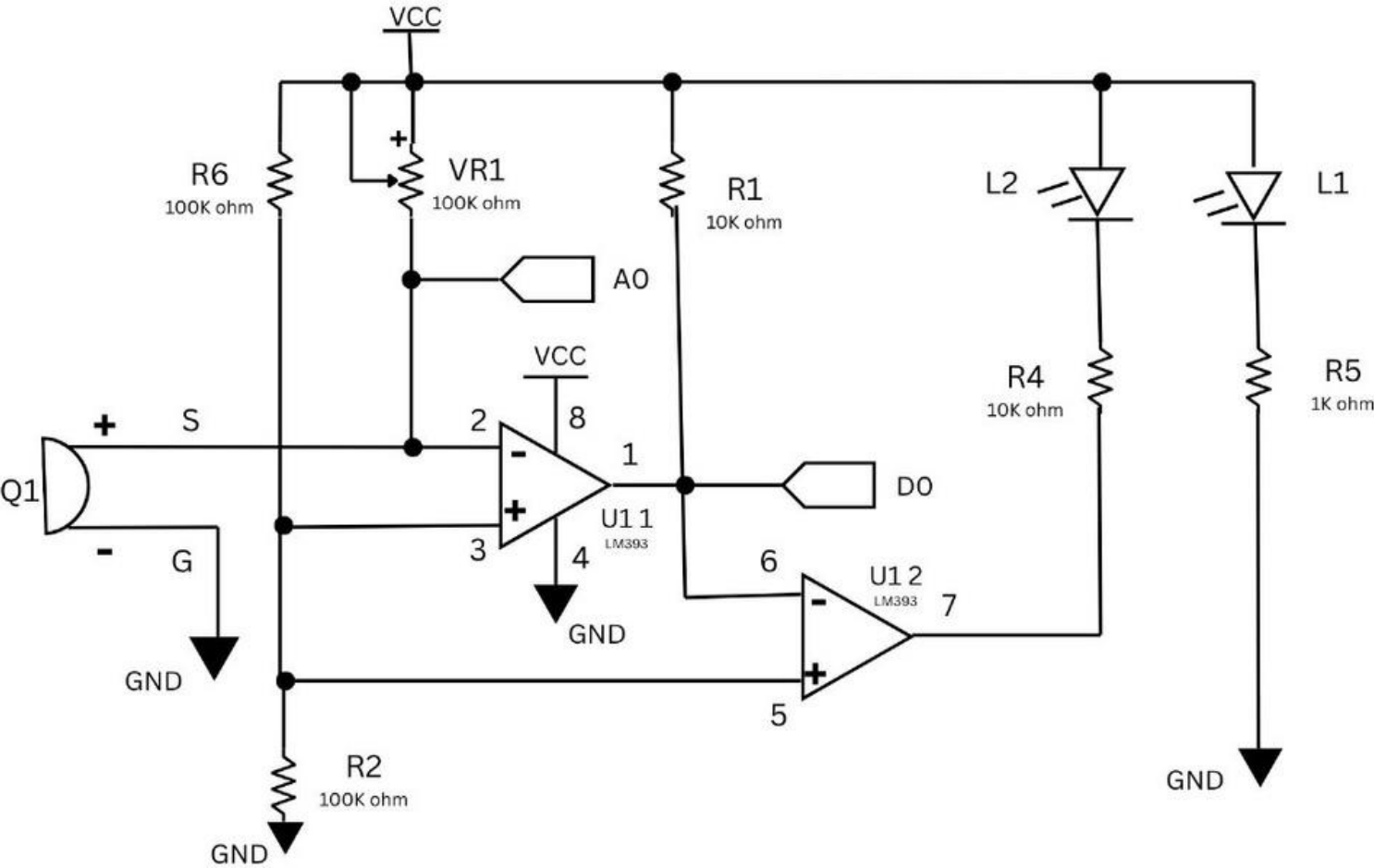

PROTOTYPE IMAGE

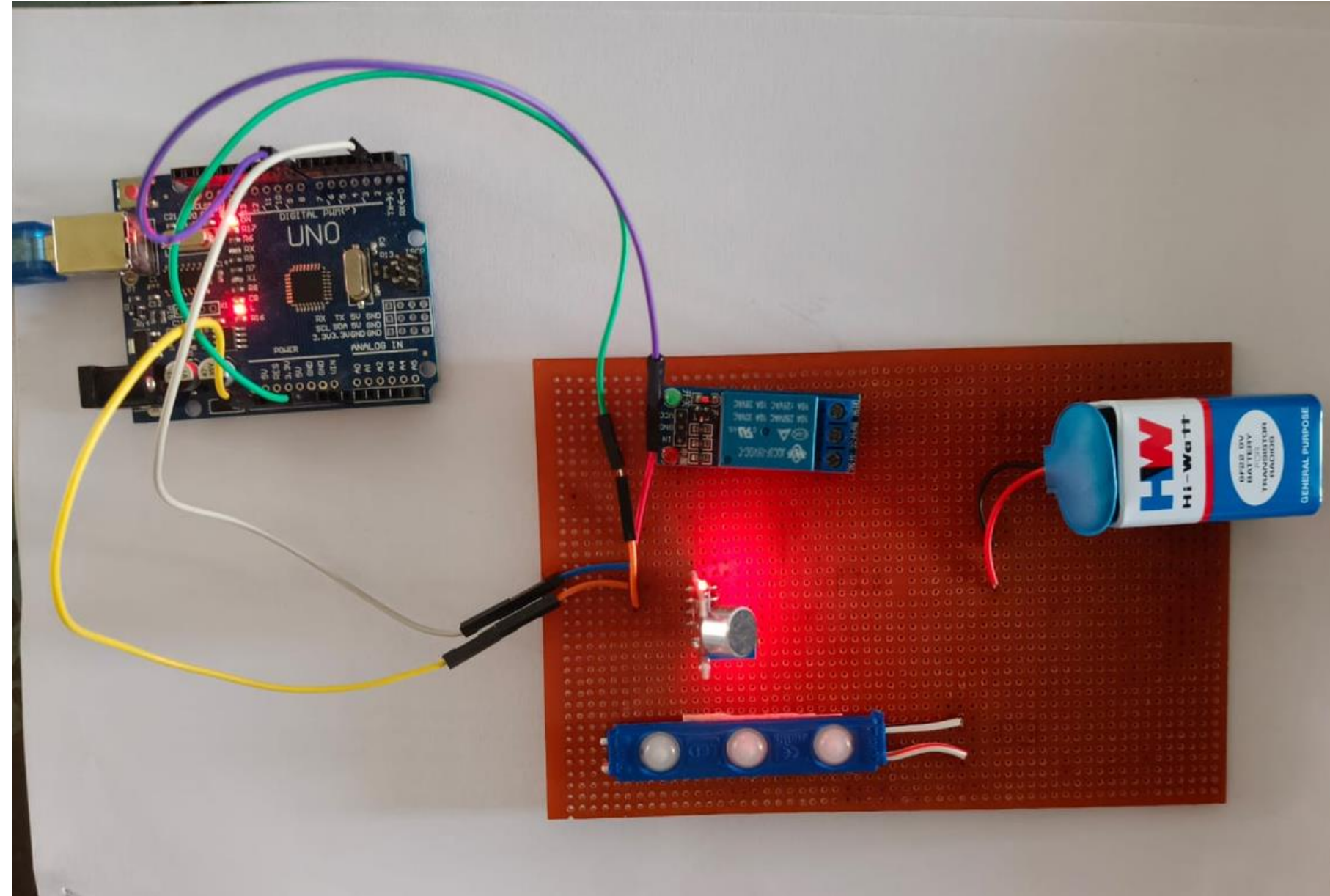

CODING

main_modified.ino

```
1  int soundSensor = 2;
2  int relayPin = 8;
3  bool relayState = false;
4  bool lastSoundState = LOW;
5  unsigned long lastToggleTime = 0;
6  int debounceDelay = 300;
7  void setup() {
8    pinMode(soundSensor, INPUT);
9    pinMode(relayPin, OUTPUT);
10   digitalWrite(relayPin, LOW);
11 }
12 void loop() {
13   bool currentSoundState = digitalRead(soundSensor);
14   unsigned long currentTime = millis();
15   if (currentSoundState == HIGH && lastSoundState == LOW && currentTime - lastToggleTime > debounceDelay)
16   {
17     relayState = !relayState; // Toggle relay state
18     digitalWrite(relayPin, relayState ? HIGH : LOW);
19     lastToggleTime = currentTime;
20   }
21   lastSoundState = currentSoundState;
22 }
23
```

WORKING PRINCIPLE


This project uses an LM393 sound sensor, Arduino, and a relay module to toggle an electrical device (like a lamp) based on sound input. The LM393 acts as a voltage comparator, comparing the amplified sound signal from the microphone to a reference voltage set by a potentiometer. When the sound signal exceeds the reference threshold, the LM393 outputs a digital HIGH signal to the Arduino. The Arduino reads this signal and toggles the relay state, turning the connected device ON or OFF. This setup enables simple sound-based automation using comparator logic.



ADVANTAGES:

- Automation – The light automatically turns ON or OFF in response to sound (like claps or voice), removing manual effort.
- Simple to Build – Easy wiring and coding make it ideal for beginners in embedded systems.
- Low Cost – Uses inexpensive components like Arduino Uno, mic sensor, and a relay module.

APPLICATIONS:

- It helps elderly or disabled people control lighting without physical touch.
 - It can be used in smart homes for clap-based automation systems.
 - Also useful in security systems where loud noise triggers lights or alarms
- 



CONCLUSION

This proposed system is affordable, reliable and easy to use.

It helps physically disabled persons to control appliances without any help.

can be further upgraded with toggle function , noise filtration , wireless communication.



THANK YOU